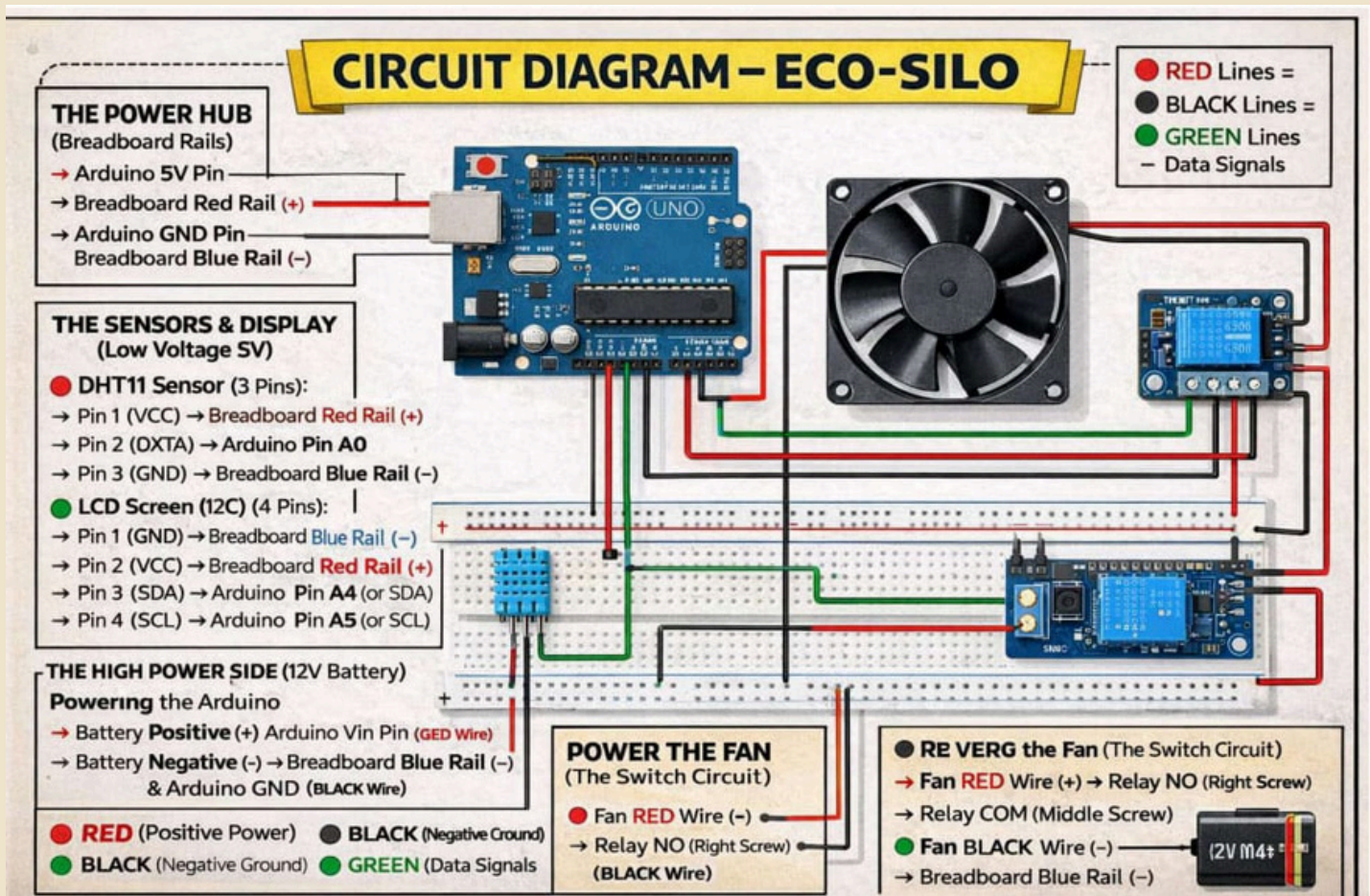


# ECO-SILO: SMART GRAIN SAVER



# Circuit details



Color Key:

- Red lines = Positive power(+)
- Black lines = Negative Ground(-)
- Green lines = Data signals

## 1. The Power Hub (Breadboard Rails)

(Think of this as your power strip)

● Arduino 5V Pin → Breadboard Red Rail (+)

● Arduino GND Pin → Breadboard Blue Rail

## 2. The sensors and display (low voltage 5V) (These plug into the breadboard rails you just powered)

### A. DHT11 Sensor (3 Pins)

● Pin 1 (VCC) → Breadboard Red Rail (+)

● Pin 2 (DATA) → Arduino Pin A0

● Pin 3 (GND) → Breadboard Blue Rail (-)

### B. LCD Screen (I2C) (4 Pins)

● Pin 1 (GND) → Breadboard Blue Rail (-)

● Pin 2 (VCC) → Breadboard Red Rail (+)

● Pin 3 (SDA) → Arduino Pin A4 (or SDA)

● Pin 4 (SCL) → Arduino Pin A5 (or SCL)

## C. Relay Module Input

● (3 Pins on the small side)

● VCC → Breadboard Red Rail (+)

● GND → Breadboard Blue Rail (–)

IN → Arduino Pin D7

## 3. The High Power Side (12V Battery)

(This is the critical part)

### A. Powering the Arduino

● Battery Positive (+) → Arduino Vin Pin

● Battery Negative (–) → Breadboard Blue Rail(–)

(This connects Battery GND to Arduino GND)

### B. Powering the Fan (The Switch Circuit)

● Battery Positive (+) → Relay COM  
(Middle Screw Terminal)

● Relay NO (Right Screw) → Fan Red Wire (+)

● Fan BLACK wire(–)→Breadboard blue rail(–)

## HOW DOES IT WORK?

- Battery sends 12V to Arduino Vin (Arduino turns on).
- Arduino sends 5V to the Breadboard Red Rail  
(LCD & Sensor turn on).
- Battery sends 12V to the Relay COM port (Waiting at the door).
- When code says Go, Relay closes the gate.
- 12V flows from COM -> NO -> Fan. Fan spins!



# ABOUT THE SMART SILO!

**PROBLEM:**Traditional silos and godowns suffer from problems like moisture damage,fungal growth, and human error, leading to heavy food grain losses.

**SOLUTION:**A Smart Silo uses sensors, automation, and real-time monitoring to overcome these problems,ensuring safe storage, reduced wastage and sustainable development.It automatically detect humidity inside the grain jar.If it gets too wet,a fan turns to dry it out.

## HOW IT HELPS?

By protecting grains for a longer time, it ensures that farmers do not lose their hard-earned produce and get better returns for their crops

For people, it means a steady supply of safe and good-quality food at affordable prices.

In situations like floods, droughts, pandemics, or emergencies, when food supply chains are disturbed, a Smart Silo feels like a god-gifted system because it preserves food securely and prevents wastage.

## Scientific Principle:

Respiration: Grains are seeds. They “breathe” like humans, releasing heat and moisture.

Hot Spot Effect: If this moisture gets trapped, fungus grows.

Convection: The project uses a fan to push fresh air through the grain, removing moisture before fungus can start.

# ABOUT THE MODEL

Materials required:

Arduino Uno R3.

DHT 22 OR DHT 11(3 PINS)

16 X 2 LCD WITH I2C MODULE

RELAY MODULE 5V, 1  
CHANNEL WITH HIGH LOW LEVEL TRIGGER

12V DC BRUSHLESS(CPU FAN) SIZE:120 MM  
JUMPER WIRES: M-M & M-F: 20 EACH.

BREADBOARD -1

12V BATTERY OR ADAPTER

BLADE TYPE 2 AMP FUSE

## Working Model:

Jar A (The “Smart” Silo): A plastic jar filled with rice/wheat. It has a DHT11 sensor inside and a fan on top.

Jar B (The “Dumb” Silo): A completely sealed jar with rice (passive control).

To simulate “bad weather” or wet grain during the demo, we place a small piece of damp sponge or wet bread inside both jars.

## Observation:

Jar B: The humidity rises and stays high (trapped). The bread inside gets moldy after 3–4 days.

Jar A: The sensor detects moisture from the wet sponge. The red light turns ON → the fan starts spinning → the LCD shows humidity dropping → the green light turns ON. The bread stays dry and fresh.